

Name: _____ ID# _____

Date Submitted: _____ Lab Section # _____

CSE 2441 – Digital Logic Design

Fall Semester 2020

Lab Number 3 – Basic Adders

Due September 20, 2020 (11:59 PM)

This exercise uses The BitBoard.

BASIC ADDERS


(100 POINTS)

PURPOSE/OUTCOMES

To introduce you to basic circuits for adding binary numbers. After completing this lab, you will have demonstrated an ability to design four-bit adders, to capture and verify your designs using Quartus II, and to construct and test your designs on a BB/DE1.

LAB REQUIREMENTS

In Lab 2, you designed and simulated a full adder and a four-bit ripple-carry adder that used four full-adders as components as shown in Figure 1. In this lab you will construct and test these circuits.

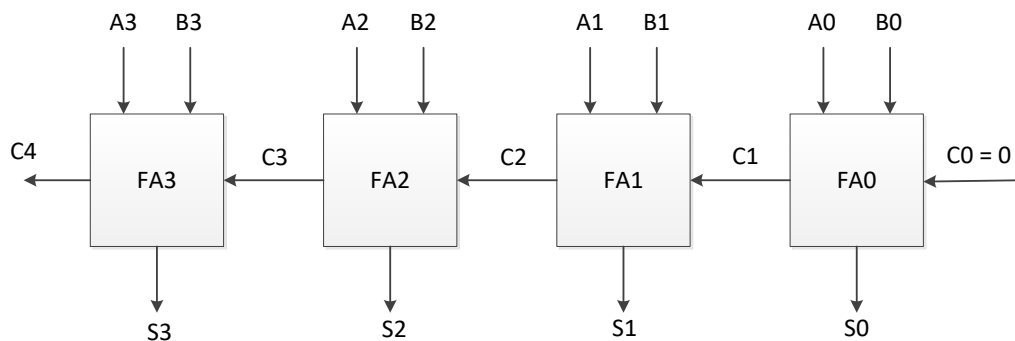Figure 1 – Four-Bit Ripple-Carry Adder ($A + B$)

1. Prove that both of the following circuits realize a full adder by constructing them on the BitBoard and experimentally deriving their truth tables. **Take pictures of your circuits and record your truth tables for your lab report.** Use the following BB/DE1 pin assignments when deriving the truth tables.

A: SW2, **B:** SW1, **C:** SW0, **S** (circuit 1): LEDR1, **Cout** (circuit 1): LEDR0,
S (circuit 2): LEDG1, **Cout** (circuit 2): LEDG0

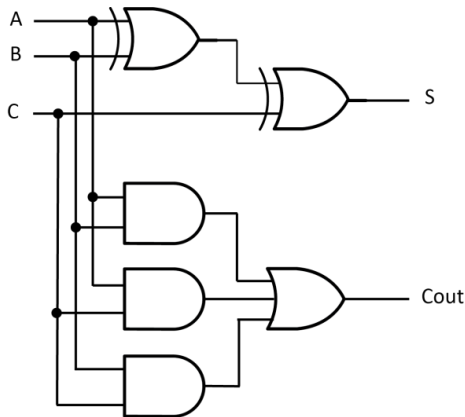


Figure 2 – Circuit 1

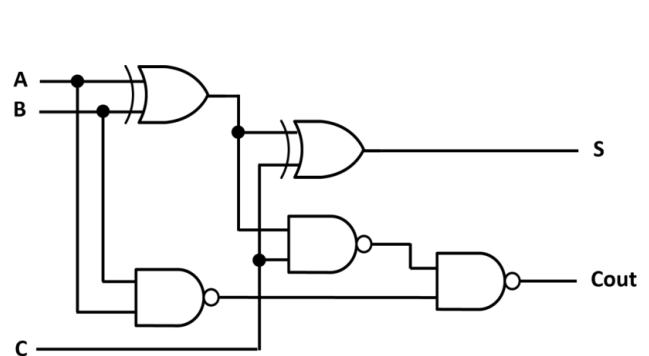


Figure 3 – Circuit 2

2. Using the simplest(fewest chips) full adder circuit from above, construct a four-bit ripple-carry adder realization as shown in Figure 1. **Note: It is wise to build and test your adder one stage at a time!** Use the following BB/DE1 pin assignments.

A3: SW7, A2: SW6, A1: SW5, A0: SW4
 B3: SW3, B2: SW2, B1: SW1, B0: SW0
 S3: LEDR3, S2: LEDR2, S1: LEDR1, S0: LEDR0
 C4: LEDR4
 C0: SW8

Take a picture of your completed circuit.

3. Test your ripple-carry adder for the values of A and B in the following table.

A	B	$S = A + B$	$Cout (C4)$
0101	0001		
0111	0001		
0111	1111		
1001	1110		
1010	1110		
1101	1100		

4. If $A3$, $B3$, and $C3$ are sign bits, do any of the above results produce an overflow?

REPORT REQUIREMENTS

1. Cover sheet (as shown on this assignment)
2. Lab purpose
3. Picture of Circuit 1
4. Truth table of Circuit 1
5. Picture of Circuit 2
6. Truth table of Circuit 2
7. Picture of Ripple-Carry Adder Circuit
8. Ripple-carry adder test results table
9. Answers to #4.

LEAVE YOUR RIPPLE-CARRY ADDER CIRCUIT ON THE BITBOARD FOR USE IN LAB #4.